

Engn
Engin
IEEE
(1974-2001)
3/16/95

RECEIVED
CENTRAL FAX CENTER

SEP 22 2005

Principles of Data Conversion System Design

Behzad Razavi
AT&T Bell Laboratories



IEEE
PRESS

BEST AVAILABLE COPY

IEEE Circuits and Systems Society, *Sponsor*

The Institute of Electrical and Electronics Engineers, Inc., New York

EN6P

TK

7887.6

.R39

1995

This book may be purchased at a discount from the publisher when ordered in bulk quantities. For more information contact:

IEEE PRESS Marketing
Attn: Special Sales
P.O. Box 1331
445 Hoes Lane
Piscataway, NJ 08855-1331
Fax: (908) 981-8062

©1995 by AT&T. All rights reserved.

All rights reserved. No part of this book may be reproduced in any form, nor may it be stored in a retrieval system or transmitted in any form, without written permission from the publisher.

Printed in the United States of America

10 9 8 7 6 5 4 3 2 1

ISBN 0-7803-1093-4

IEEE Order Number: PC4465

Library of Congress Cataloging-in-Publication Data

Razavi, Behzad.

Principles of data conversion system design / Behzad Razavi.
p. cm.

Includes bibliographical references and index.

ISBN 0-7803-1093-4

1. Analog-to-digital converters—design and construction.
2. Digital-to-analog converters—Design and construction.
3. Integrated circuits—Design and construction. I. Title.

TK7887.6.R39 1995

621.39'814—dc20

94-26694

CIP

Contents

PREFACE *xi*

CHAPTER 1 INTRODUCTION TO DATA CONVERSION AND PROCESSING 1

CHAPTER 2 BASIC SAMPLING CIRCUITS 7

- 2.1 General Considerations 7
- 2.2 Performance Metrics 11
- 2.3 Sampling Switches 13
 - 2.3.1 MOS Switches 14
 - 2.3.2 Diode Switches 19
 - 2.3.3 Comparison of MOS and Diode Switches 23
 - 2.3.4 Improvements in MOS Switch Performance 24
- References 27

CHAPTER 3 SAMPLE-AND-HOLD ARCHITECTURES 29

- 3.1 Conventional Open-Loop Architecture 29
- 3.2 Conventional Closed-Loop Architecture 31
- 3.3 Open-Loop Architecture with Miller Capacitance 33

- 3.4 Multiplexed-Input Architectures 35
- 3.5 Recycling Architecture 39
- 3.6 Switched-Capacitor Architecture 40
- 3.7 Current-Mode Architecture 42
- References 43

CHAPTER 4 BASIC PRINCIPLES OF DIGITAL-TO-ANALOG CONVERSION 45

- 4.1 General Considerations 45
- 4.2 Performance Metrics 47
- 4.3 Reference Multiplication and Division 49
 - 4.3.1 Voltage Division 50
 - 4.3.2 Current Division 55
 - 4.3.3 Charge Division 63
- 4.4 Switching and Logical Functions in DACs 70
 - 4.4.1 Switching Functions in Resistor-Ladder DACs 70
 - 4.4.2 Switching Functions in Current-Steering DACs 72
 - 4.4.3 Switching Functions in Capacitor DACs 74
 - 4.4.4 Binary-to-Thermometer Code Conversion 76
- References 77

CHAPTER 5 DIGITAL-TO-ANALOG CONVERTER ARCHITECTURES 79

- 5.1 Resistor-Ladder DAC Architectures 79
 - 5.1.1 Ladder Architecture with Switched Subdivider 79
 - 5.1.2 Intermeshed Ladder Architectures 82
- 5.2 Current-Steering Architectures 84
 - 5.2.1 R - $2R$ -Network Based Architectures 84
 - 5.2.2 Segmented Architectures 90
- References 94

CHAPTER 6 ANALOG-TO-DIGITAL CONVERTER ARCHITECTURES 96

- 6.1 General Considerations 96
- 6.2 Performance Metrics 99
- 6.3 Flash Architectures 101
 - 6.3.1 Reference Ladder DC and AC Bowing 103
 - 6.3.2 Nonlinear Input Capacitance 106

Contents

Contents

ix

DACs 70
 DACs 72
 74
 n 76

URES 79

livider 79

URES 96

103

- 6.3.3 Kickback Noise 107
- 6.3.4 Sparkles in Thermometer Code 108
- 6.3.5 Metastability 110
- 6.3.6 Slew-Dependent Sampling Point 112
- 6.3.7 Clock Jitter and Dispersion 112
- 6.3.8 Gray Encoding 114
- 6.4 Two-Step Architectures 116
 - 6.4.1 Effect of Nonidealities 121
 - 6.4.2 Two-Step Recycling Architecture 124
 - 6.4.3 Two-Step Subranging Architecture 125
- 6.5 Interpolative and Folding Architectures 126
 - 6.5.1 Interpolation 127
 - 6.5.2 Folding Architectures 132
 - 6.5.3 Folding with Interpolation 136
- 6.6 Pipelined Architectures 140
- 6.7 Successive Approximation Architectures 143
- 6.8 Interleaved Architectures 147
- References 149

CHAPTER 7 BUILDING BLOCKS OF DATA CONVERSION SYSTEMS 153

- 7.1 Amplifiers 153
 - 7.1.1 Open-Loop Amplifiers 153
 - 7.1.2 Closed-Loop Amplifiers 160
 - 7.1.3 Operational Amplifiers 164
 - 7.1.4 Gain Boosting Techniques 171
 - 7.1.5 Common-Mode Feedback 172
- 7.2 Comparators 177
 - 7.2.1 Bipolar Comparators 181
 - 7.2.2 CMOS Comparators 188
 - 7.2.3 BiCMOS Comparators 191
- References 195

CHAPTER 8 PRECISION TECHNIQUES 198

- 8.1 Comparator Offset Cancellation 198
 - 8.1.1 Input Offset Storage 199
 - 8.1.2 Output Offset Storage 201
 - 8.1.3 Multistage Offset Storage 202
 - 8.1.4 Comparators Using Offset-Cancelled Latches 206
- 8.2 Op Amp Offset Cancellation 208

x

Contents

8.3	Calibration Techniques	211
8.3.1	DAC Calibration Techniques	211
8.3.2	ADC Calibration Techniques	218
8.4	Range Overlap and Digital Correction	224
	References	229

CHAPTER 9 TESTING AND CHARACTERIZATION 232

9.1	General Considerations	232
9.2	Sampling Circuits	234
9.3	D/A Converters	239
9.4	A/D Converters	239
9.4.1	Static Testing	239
9.4.2	Dynamic Testing	241

INDEX 252

**This Page is Inserted by IFW Indexing and Scanning
Operations and is not part of the Official Record**

BEST AVAILABLE IMAGES

Defective images within this document are accurate representations of the original documents submitted by the applicant.

Defects in the images include but are not limited to the items checked:

- ☒ **BLACK BORDERS**
- ☐ **IMAGE CUT OFF AT TOP, BOTTOM OR SIDES**
- ☐ **FADED TEXT OR DRAWING**
- ☐ **BLURRED OR ILLEGIBLE TEXT OR DRAWING**
- ☐ **SKEWED/SLANTED IMAGES**
- ☒ **COLOR OR BLACK AND WHITE PHOTOGRAPHS**
- ☐ **GRAY SCALE DOCUMENTS**
- ☐ **LINES OR MARKS ON ORIGINAL DOCUMENT**
- ☒ **REFERENCE(S) OR EXHIBIT(S) SUBMITTED ARE POOR QUALITY**
- ☐ **OTHER:** _____

IMAGES ARE BEST AVAILABLE COPY.

As rescanning these documents will not correct the image problems checked, please do not report these problems to the IFW Image Problem Mailbox.